

Questions:

Draw the truth table for a 3-input LUT.

Using 2:1 multiplexers, draw the circuit for 3-input LUT.

How many programming function bits are required for a 3-input LUT?

What is a bitstream file used for?